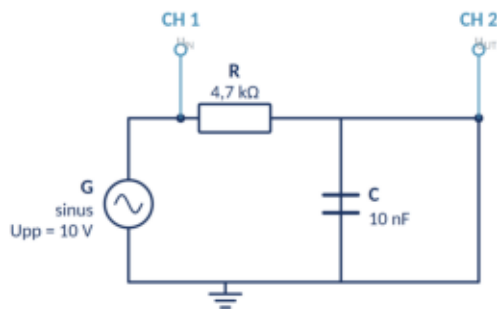


Jméno: _____ Skupina: _____ Datum: _____



Vztahy

$$f_M = 1 / (2\pi \cdot R \cdot C)$$

$$A_u = 20 \cdot \log (U_{out} / U_{in})$$

$$R = 4,7 \text{ k}\Omega \quad C = 10 \text{ nF}$$

$$f_M \text{ výpočet} = \text{_____ Hz}$$


$$f_M \text{ z grafu } (-3 \text{ dB}) = \text{_____ Hz}$$

f [Hz]	U _{in} (pp) [V]	U _{out} (pp) [V]	A _u [dB]	φ [°]
100				
200				
500				
1 000				
2 000				
3 390				
5 000				
10 000				
20 000				
50 000				
100 000				

Amplitudová charakteristika



Fázová charakteristika

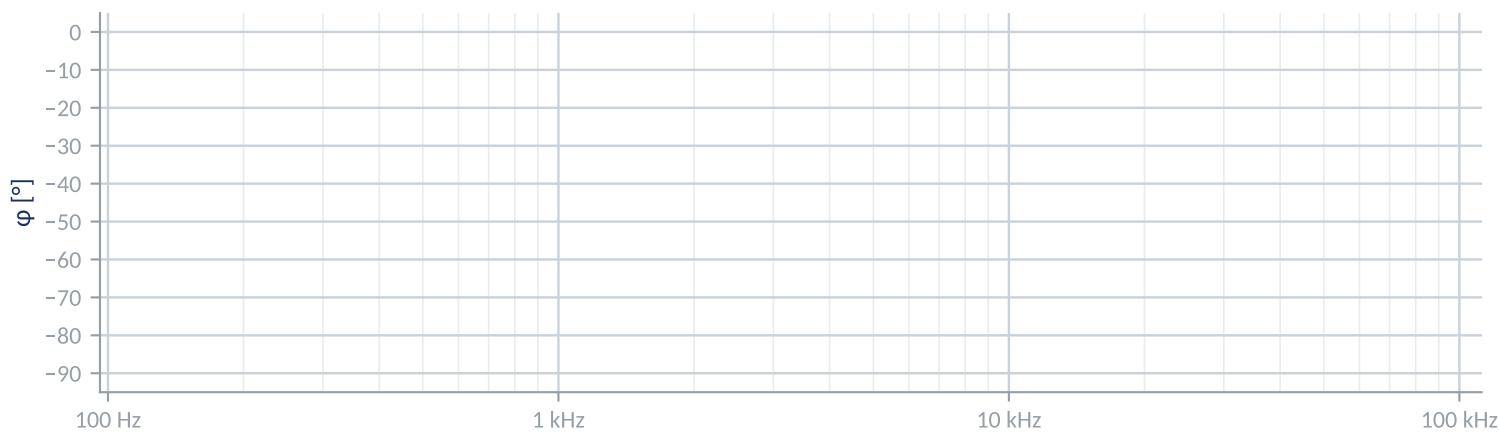


frekvence

Jméno: _____

Skupina: _____

Datum: _____

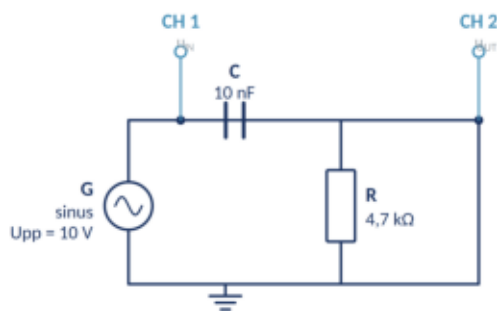**Vztahy**

$$f_M = 1 / (2\pi \cdot R \cdot C)$$


$$A_u = 20 \cdot \log (U_{out} / U_{in})$$

$$R = 4,7 \text{ k}\Omega \quad C = 10 \text{ nF}$$

$$f_M \text{ výpočtem} = \text{_____ Hz}$$

$$f_M \text{ z grafu } (-3 \text{ dB}) = \text{_____ Hz}$$

f [Hz]	U _{in} (pp) [V]	U _{out} (pp) [V]	A _u [dB]	φ [°]
100				
200				
500				
1 000				
2 000				
3 390				
5 000				
10 000				
20 000				
50 000				
100 000				

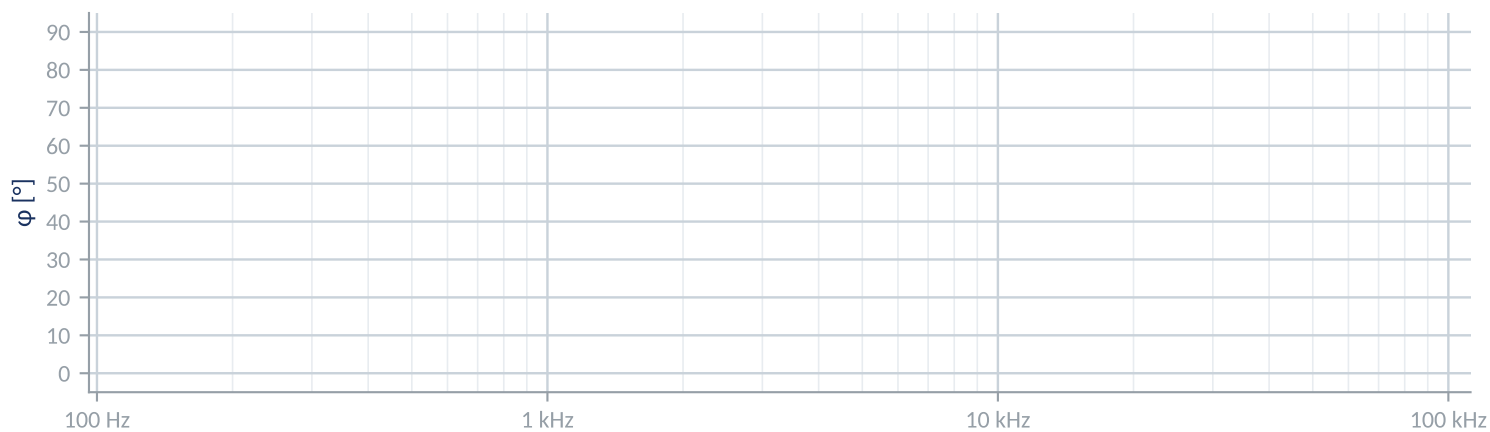Amplitudová charakteristika**Fázová charakteristika**

frekvence